

EST526 Final Project Report.

1. Summary.

1.1 Algorithmic Simplification.

$$F(x) = \frac{ax+b}{cx+d}$$

$$= \frac{a}{c} + \left(\frac{b}{c} - \frac{ad}{c^2}\right) \frac{1}{x + \frac{d}{c}}$$

$$-1 < x < 1.$$

1.2 numerical to physical values mapping.

The specifications of parameters are:

$$\textcircled{1} a, b, c, d \in \mathbb{R}$$

$$\textcircled{2} x \in \mathbb{R}, -1 < x < 1.$$

Because $F(x)$ is calculated by physical values, it can't be infinity, thus $1 = \frac{d}{c}$ or $\frac{d}{c} < -1$

Another specification is $c \neq 0$; other wise

$$F(x) = \frac{a}{d}x + \frac{b}{d} \text{ is easy to implement.}$$

To make physical values are ~~handet~~ handled by transistors properly, a mapping:

$$G(a) = a \cdot I_{ref}$$

is designed assigned.

Thus the actual function performed is

$$\frac{G(a)}{G(c)} + \left(\frac{G(b)}{G(c)} - \frac{G(a)G(d)}{G(c)^2} \right) \frac{1}{x + \frac{G(d)}{G(c)}}$$

$$G(F(x)) = \frac{G(a)}{G(c)} I_{ref} + \left(\frac{G(b)}{G(c)} - \frac{G(a)G(d)}{G(c)^2} \right) \frac{I_{ref}}{G(x) + \frac{G(d)I_{ref}}{G(c)}} \quad (1)$$

Equation (1) is implemented through circuit.

$G(a)$ are presented by currents.

1.3. Design Specifications.

From Equ. (1) and Mapping $G(a)$ we know that

$$G(-a) = -G(a)$$

and the direction of currents can be changed according to current's positively or negatively.

Thus we can assume that

$$a, b, c, d > 0$$

$$\text{and } \frac{c}{d} > 1.$$

Other conditions ~~are~~ can be handled in some way.

rather than change some direction of currents.

1.4. Choice of I_{ref}

I_{ref} is chosen to make all the values in circuits work in designed condition.

In this project, sub-threshold mode is used, n_{mos}

$$I \propto \frac{d}{L} \frac{1}{e^{V_{gs}/V_t}}$$

$$I \propto e^{V_{gs}/V_t} \text{ when } w = 6 \mu m, l = 3 \mu m.$$

in the region of

$$20 pA < I < 12 nA.$$

$$0.3V < V_{gs} < 0.6V$$

$$V_{as} > V_{Th}.$$

Thus I_{ref} is chosen according to

$$\frac{G(a)}{G(c)}, \frac{G(b)}{G(c)}, \frac{G(a)G(d)}{G(c)^2}, G(x) + \frac{G(d)}{G(c)} I_{ref}, \frac{G(d)}{G(c)}$$

and $G(a), G(b), G(c), G(d)$ in region of

$$[20 pA, 12 nA].$$

In later section of experiment,

$$I_{ref} = 1 nA, a = 1, b = 2, c = 5, d = 12.$$

2. Circuit Schematic.

2.1. Calculation.

 


Fig 1: Simplified calculation.

$$I_1 = \left[\frac{G(a)G(d)}{G(c)} - \frac{G(b)}{G(c)} \right] I_{ref} = 0.08 \text{ nA}.$$

$$I_2 = \frac{G(d)}{G(c)} I_{ref} = 2.4 \text{ nA}.$$

$$I_4 = \frac{G(a)}{G(c)} I_{ref} = 0.4 \text{ nA}. \quad I_3 = X \cdot I_{ref} = G(x).$$

$$R = 10 \text{ k}\Omega.$$

We can check that

$$I_{out} = G(F(x)) = F(x) \cdot I_{ref}.$$

I_1, I_2, I_4 don't depend on x , can be assigned in simulation.

2.2. Fixed-point schematic.

 


Fig 2: Simplified fixed-point calculation.

A great point of that design is we don't need to worry about stability issue in fixed-point feedback. because there are 2 poles in changing feedback and a ~~right~~ right hand zero, it is easy to do frequency compensation by.

adding miller capacitor from p_1 to p_2 .

In this simulation, no problem of stability is met.

2.3. Full design

Fig 3 shows a multiplier & Divider.

 


Fig 3.

We can show that $I_4 = \frac{I_1 I_2}{I_3}$.

Thus,

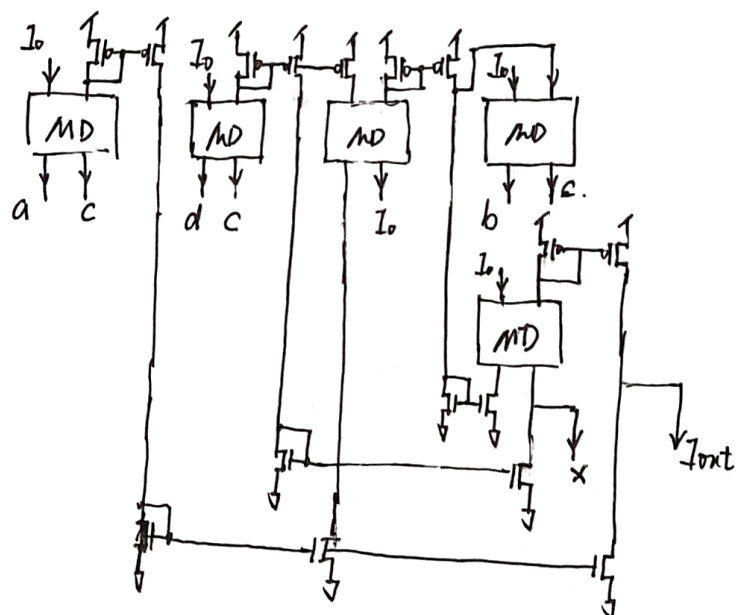


Fig 4: Full Design. $I_0 = I_{ref}$.

Fig 4 shows a full design, which take a, b, c, d, x as input, and I_{out} as output.

3b transistor.